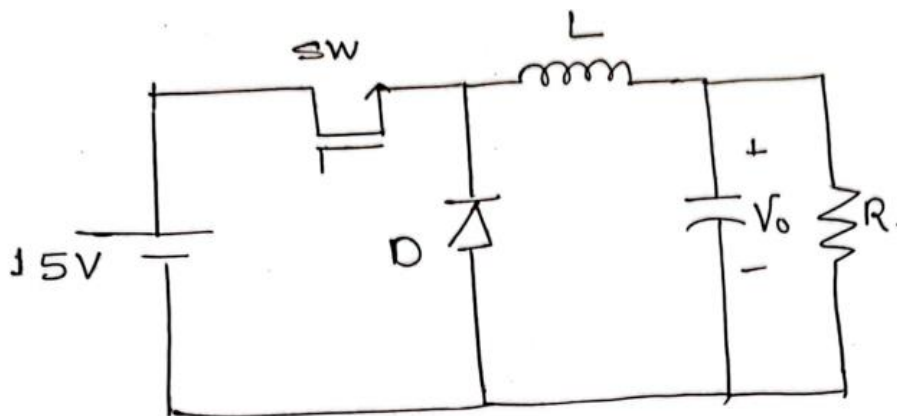



Assignment 2 (EE 238)

1. Design a buck converter with a source voltage of 50 V and duty ratio of 0.6. The load resistance is $20\ \Omega$. The maximum voltage ripple in the capacitor is 1% of the average capacitor voltage and the maximum ripple current is 5% of the average output current. Assume the converter is operating in CCM (Continuous Conduction Mode). The switching frequency is 2 kHz. **(Ans: $L=80\text{ mH}$; $C=15.625\ \mu\text{F}$)**

2. Find the output voltage of the following circuit considering the forward voltage drop of the MOSFET as 1 V and the forward voltage drop of the diode as 0.7 V. The switch is ON for 40% of the time in a switching cycle. The switching frequency is 5 kHz and assume CCM. **(Ans: $V_o=5.18\text{ V}$)**



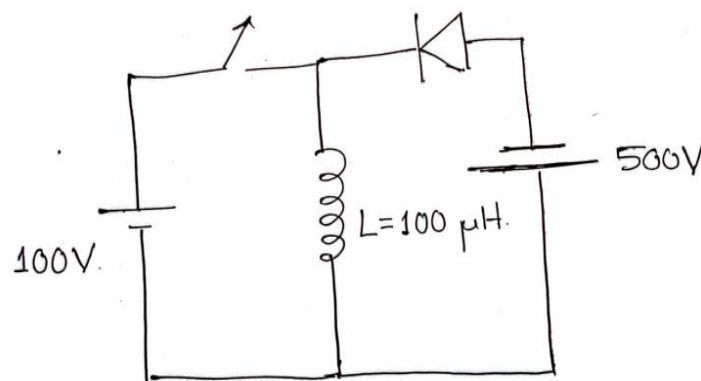3. Consider the following circuit. The $f_s=10\text{ kHz}$ of the switch.



The minimum current of the inductor is zero but never for a finite duration at the steady state. Find the peak value of the inductor current and also the duty ratio.
(Ans: $I_{L,pk}=83.33\text{ A}$; $D=5/6$)

4. For a buck converter, the source voltage is 100 V, the duty ratio is 0.4 and the output voltage is 50 V. Given $L=200\text{ }\mu\text{H}$ and $f_s=20\text{ kHz}$, find


a) the peak value of the current.

b) The average output current.

(Ans: $I_{L,pk}=5\text{ A}$, $I_0=2\text{ A}$)

5. Assuming CCM, draw the waveforms of the switch current, diode current, inductor current and the capacitor current for both Boost and Buck-Boost converters.

Ans. 1)

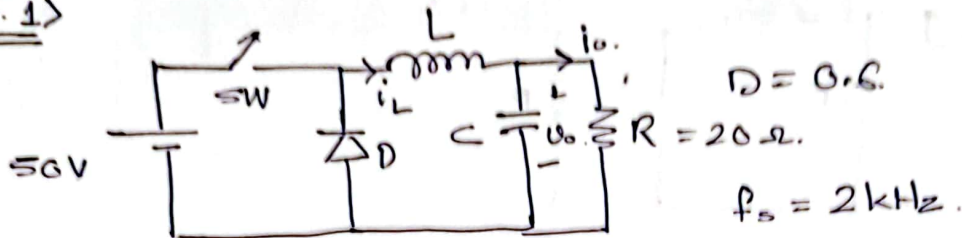

$$\Delta V_c = 0.01 V_o \quad \text{--- (1)}$$

$$V_o = D V_{dc} = 0.6 \times 50 = 30 \text{ V} \quad \text{--- (2)}$$

$$\Delta V_c = 0.01 \times 30 = 0.3 \text{ V} \quad \text{--- (3)}$$

$$\Delta V_c = \frac{\Delta I_L}{8C} \quad \text{--- (4)}$$

$$I_o = I_L = \frac{30}{20} = 1.5 \text{ A} \quad \text{--- (5)}$$

$$\Delta I_L = \frac{V_o(1-D)T_s}{L} \quad \text{--- (6)}$$

$$0.05 \times 1.5 = \frac{30 \times 0.4}{2 \text{ k} \times L}$$



$$\Rightarrow \boxed{L = \frac{12}{1.5 \times 0.05 \times 2 \text{ k}} = 80 \text{ mH}} \quad \text{--- (1)}$$

$$C = \frac{\Delta I_L T_s}{\Delta V_c \times 8} = \frac{0.05 \times 1.5}{8 \times 0.01 \times 30 \text{ f}_s}$$

$$= \frac{5 \times 1.5}{240 \times 2 \text{ k}}$$

$$\Rightarrow \boxed{C = 15.625 \mu\text{F}} \quad \text{--- (2)}$$

2)

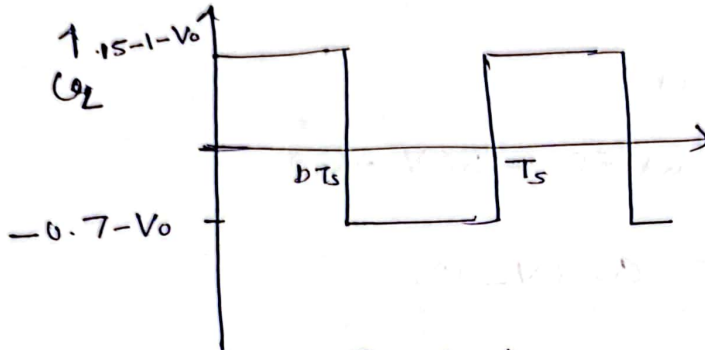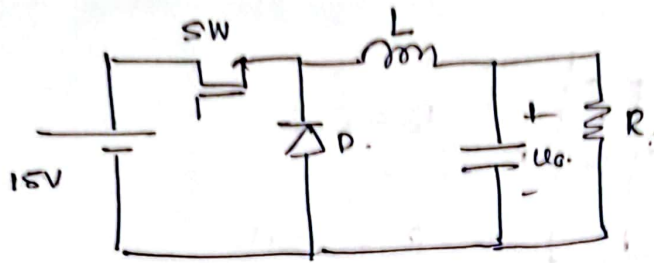

$$D = 0.4$$

$$\langle u_o \rangle = 0 \Rightarrow (15 - 1 - V_o) D T_s = (+0.7 + V_o) (1 - D) T_s$$

$$\Rightarrow (14 - V_o) \times 0.4 = (+0.7 + V_o) \times 0.6$$

$$\Rightarrow 5.6 - 0.4V_o = +0.42 + 0.6V_o$$

$$\Rightarrow -0.2V_o = -5.58$$

\Rightarrow

$$V_o =$$

\Rightarrow


$$55.58 = V_o$$

$$\therefore V_o = 55.58 \text{ V.}$$


\Rightarrow

$$V_o = 5.18 \text{ V}$$

Ans 3.

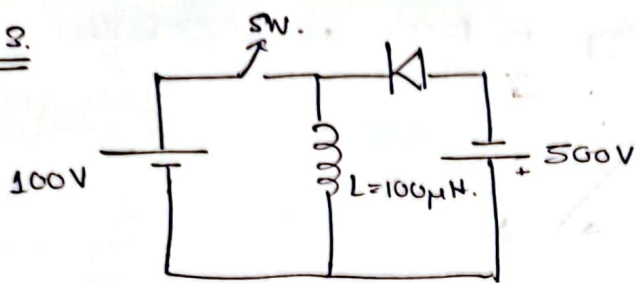

$$f_s = 10 \text{ kHz}$$

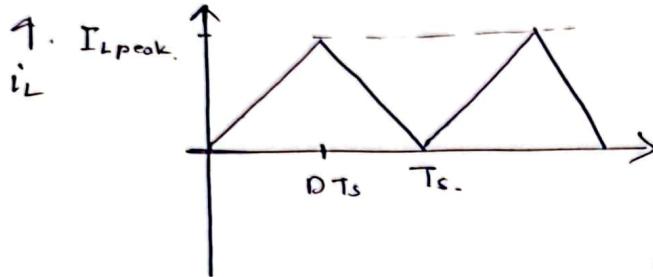

$$\frac{100}{L} \times DT_s = (1-D)T_s \times \frac{500}{L}$$

$$\Rightarrow 5 = \frac{D}{1-D}$$

$$\Rightarrow \boxed{D = \frac{5}{6}} \quad (1)$$


$$\begin{aligned} \therefore I_{L, \text{peak}} &= \frac{100 \times DT_s}{L} \\ &= \frac{100}{100 \mu} \times \frac{5}{6} \times \frac{1}{10^4} \end{aligned}$$

$$\boxed{I_{L, \text{peak}} = 83.33 \text{ A}}$$

$$\begin{aligned} I_{L, \text{peak}} &= \frac{100 \times DT_s}{L} \\ &= \frac{100}{100 \mu} \times \frac{5}{6} \times \frac{1}{10^4} \end{aligned}$$


$$\boxed{I_{L, \text{peak}} = 83.33 \text{ A}}$$

Ans. 4).

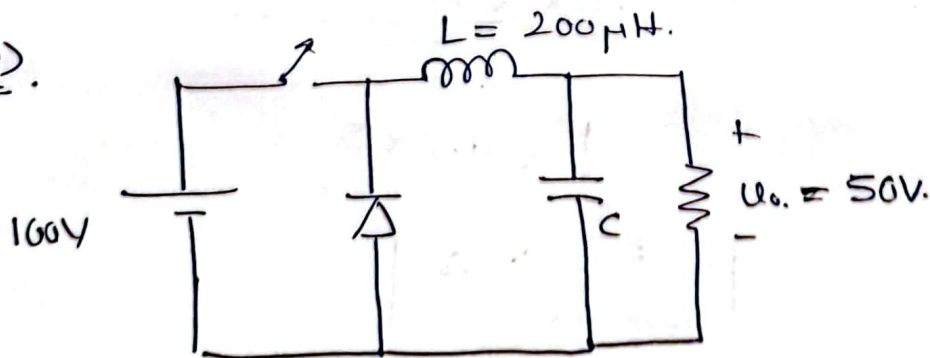

$$D = 0.4$$

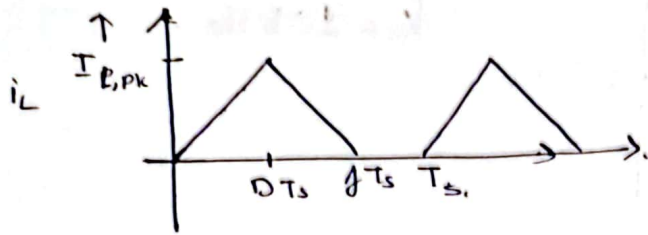The circuit is operating in DCM as $V_a > DV_{dc}$.



$$\frac{50}{100} = \frac{D}{f}$$

$$\Rightarrow f = \frac{D \times 100}{50}$$

$$= \frac{0.4 \times 100}{50}$$

$$\boxed{f = 0.8} \quad (1)$$

a) $I_{L,peak} = \left(\frac{V_{dc} - V_a}{L} \right) D T_s$

$$= \frac{(100 - 50)}{200 \mu} \times 0.4 \times 20 \text{ K}$$

$$\boxed{I_{L,peak} = \frac{50 \times 0.4}{4000 \mu \text{ s}} = \frac{20}{4} = 5 \text{ A.}}$$

b) $I_o = \langle i_L \rangle = \frac{1}{2} \times \frac{f T_s \times I_{L,peak}}{T_s}$

$$= \frac{1}{2} \times 0.8 \times 5$$

$$\boxed{I_o = 2 \text{ A.}}$$