



Assignment 4 (EE 238)

1. A single phase full bridge inverter has a switching sequence that produces a square wave voltage across a series RL load. The switching frequency is 60 Hz, $V_{dc}=100$ V, $R=10\ \Omega$ and $L=25$ mH. Determine (a) an expression for load current at steady state, (b) the power absorbed by the load, and (c) the average current in the dc source. **(Ans: (b) 441 W (c) 4.41 A)**
2. Find the relation between modulation signal $m(t)$ and the duty ratio $d(t)$. Assume $|m(t)| < 1$ and $c(t)$ is a triangular wave swinging from -1 to +1. The frequency f_c of the $c(t)$ is assumed to be very large such that $m(t)$ is assumed to be constant over one period of $c(t)$. $d(t)$ is the ratio of on time period and $1/f_c$, corresponding to the switching function $s(t)$. The switching function $s(t)$ is defined as

$$s(t)=1, \text{ when } m(t)>c(t) \\ 0 \text{ otherwise .}$$

$$\text{(Ans: } m(t)=2.d(t)-1\text{)}$$

3. Consider the following single phase full bridge inverter. The switching is defined by the switching functions defined below. Prove that the average value of v_o over one time period of $c(t)$ is $m.V_{dc}.\sin(\omega t)$ where $|m| < 1$.

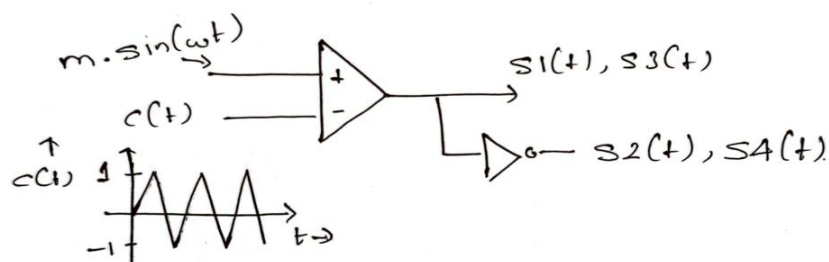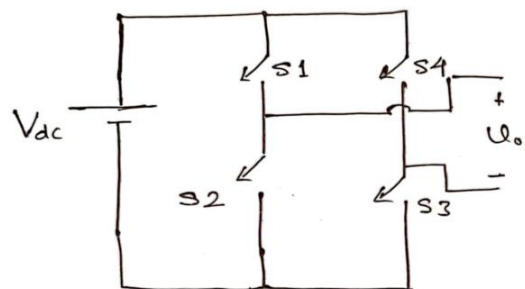

4. A three-phase full bridge inverter delivers power to a resistive load from a 450 V dc source. For a star connected load of $10\ \Omega$ per phase, determine for 180° conduction mode, (a) rms value of load current, (b) rms value of switch current and (c) load power. **(Ans: (a) 21.213 A (b) 15 A (c) 13.5 kW)**
5. A 3-ph inverter is controlled in the 180 deg conduction mode for each switch, without PWM. The fundamental inverter output frequency is $\omega = 100\pi$ radians per second. A balanced three phase star connected load is connected to the output. The load in each phase is made up of a series connection of resistor(R) and inductor(L), such that $\omega L \gg R$. If the amplitude of the 50 Hz component of the load current in each phase is 100 A, what is the amplitude of the 250 Hz current component?
(Ans: 4 A)

ASSIGNMENT-4 (EE-238)

Q1: a) $T = 1/f = 1/60 = 0.0167s$.

$\tau = L/R = 0.025/10 = 0.0025s$.

$T/2\tau = 3.33$.

$I_{\max} = -I_{\min} = \frac{V_{dc}}{R} \left(\frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right)$

$= \frac{100}{10} \left(\frac{1 - e^{-3.33}}{1 + e^{-3.33}} \right) = 9.31A$.

$i_o(t) = \frac{100}{10} + \left(-9.31 - \frac{100}{10} \right) e^{-t/0.0025}$

$i_o(t) = 10 - 19.31e^{-t/0.0025} \quad 0 \leq t \leq 1/120$

$= -10 + 19.31e^{-(t - 0.00835)/0.0025}$

$1/120 \leq t \leq 1/60$

$\therefore i_o(t) = \begin{cases} \frac{V_{dc}}{R} + (I_{\min} - \frac{V_{dc}}{R})e^{-t/\tau} & t < T/2 \\ -\frac{V_{dc}}{R} + (I_{\max} + \frac{V_{dc}}{R})e^{-(t-T/2)/\tau} & T/2 < t < T \end{cases}$

$\bullet T/2 < t < T$

b) $I_{rms} = \sqrt{\frac{1}{120} \int_0^{1/120} [10 - 19.31e^{-t/0.0025}]^2 dt}$

$= 6.64A$.

$P = I_{rms}^2 R = (6.64)^2 \times 10 = 441W$.

c) Average source current can be computed by equating source and load power.


$I_s = \frac{P_{dc}}{V_{dc}} = \frac{441}{100} = 4.41A$.

Q2:-

$$m_a(t) = \frac{V_r(t)}{C_t}$$

$$m_f = \frac{f_c}{f_r}$$

m_f is large.
 $m_a \leq 1$.

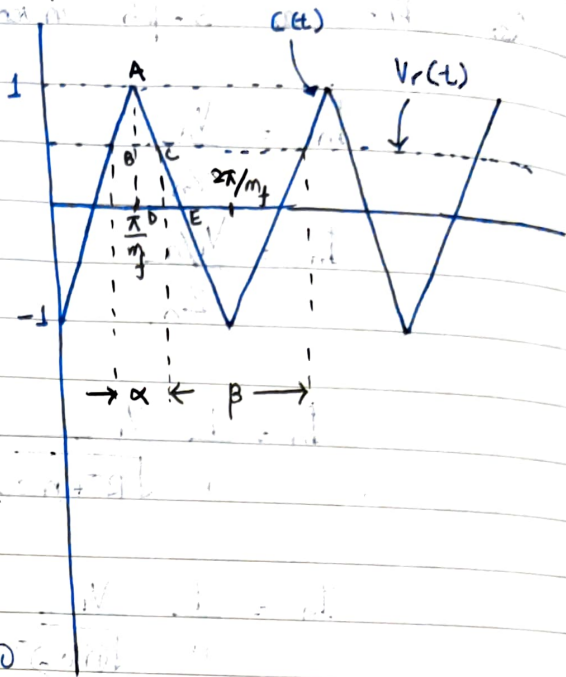

Using similarity property of triangles, in triangle $\triangle ABC$ and $\triangle ADE$

$$\frac{\alpha/2}{\pi/(2m_f)} = \frac{C_t - V_r(t)}{C_t} = \frac{C_t - m_a(t)C_t}{C_t}$$

$$\alpha = (1 - m_a) \frac{\pi}{m_f}$$

$$\text{and } \beta = \frac{2\pi}{m_f} - \alpha = (1 + m_a) \frac{\pi}{m_f}$$

The duty ratio $d(t)$ is

$$d(t) = \frac{\beta}{2\pi/m_f} = (1 + m_a(t)) \frac{\pi}{m_f} \times \frac{m_f}{2\pi}$$

$$d(t) = \frac{1}{2} (1 + m_a(t))$$

$$m_a(t) = 2d(t) - 1$$

Q8:-

$$V_o = +V_{dc}$$

$$V_o = -V_{dc}$$

$$S_1 - S_2$$

ON

$$S_3 - S_4$$

ON

The average value of V_o over one carrier cycle T_c is

$$\bar{V}_o = \frac{1}{T_c} \int_0^{T_c} V_o(t) dt$$

Since

$$V_o = +V_{dc}$$

for DT_c

$$= -V_{dc}$$

for $(1-D)T_c$

$$\bar{V}_o = \frac{1}{T_c} \left[\int_0^{DT_c} V_{dc} dt + \int_{DT_c}^{T_c} (-V_{dc}) dt \right]$$

On simplifying,

$$\bar{V}_o = (2D-1)V_{dc}$$

In Sinusoidal PWM, the duty cycle D is varied sinusoidally.


$$D = \frac{1}{2} (1 + m \sin(\omega t))$$

Substituting this into V_o ,

$$\bar{V}_o = \left(2 \times \frac{1}{2} (1 + m \sin \omega t) - 1 \right) V_{dc}$$

$$\Rightarrow \boxed{\bar{V}_o = m V_{dc} \sin \omega t}$$

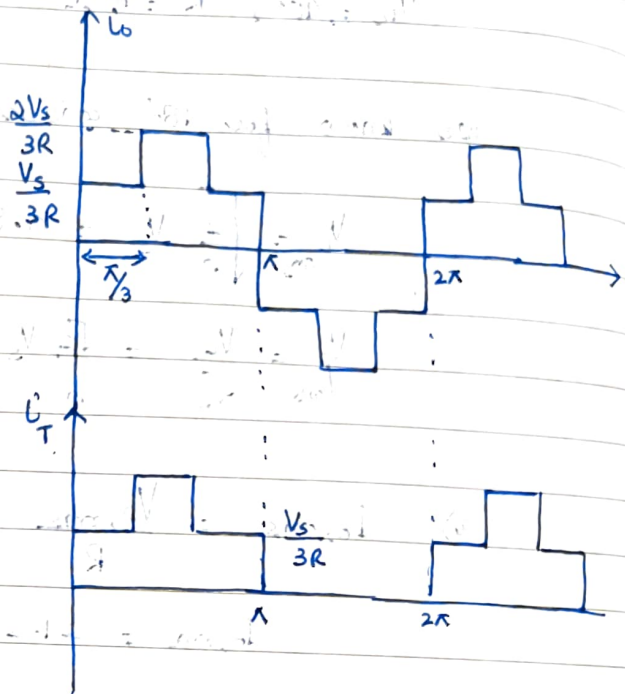Q4:- For a resistive load, waveforms of phase-load current and thyristors current are shown.



$$I_{o,rms} = \left[\frac{1}{\pi} \left[\left(\frac{V_s}{3R} \right)^2 \frac{\pi}{3} + \left(\frac{2V_s}{3R} \right)^2 \times \frac{\pi}{3} + \left(\frac{V_s}{3R} \right)^2 \frac{\pi}{3} \right] \right]^{\frac{1}{2}}$$

$$= \left[\left(\frac{450}{3 \times 10} \right)^2 \times \frac{2}{3} + \left(\frac{2 \times 450}{3 \times 10} \right)^2 \times \frac{1}{3} \right]$$

$$= \sqrt{450} = 21.213 \text{ A.}$$

$$I_{T,rms} = \left[\frac{1}{2\pi} \left\{ \left(\frac{450}{3 \times 10} \right)^2 \times \frac{2\pi}{3} + \left(\frac{2 \times 450}{3 \times 10} \right)^2 \times \frac{\pi}{3} \right\} \right]^{\frac{1}{2}}$$

$$= \sqrt{225} = 15 \text{ A.}$$

Power delivered to load

$$= 3 I_{o,rms}^2 R$$

$$= 3 \times 21.213^2 \times 10$$

$$= 13.5 \text{ kW.}$$

Qs: For a 3-ph inverter without PWM.

$$I_n = \frac{V_n}{Z_n}$$

$$I_n = \frac{V_i/n}{Z_n}$$

$$I_n = \frac{1}{n} \frac{V_i}{\sqrt{R^2 + (n\omega L)^2}}$$

$$I_n = \frac{1}{n} \frac{V_i}{\sqrt{(n\omega L)^2 + R^2}} \quad \because \omega L \gg R$$

$$= \frac{1}{n^2} \frac{V_i}{\omega L}$$

$$= \frac{1}{n^2} \times I_1$$

$$I_n = \frac{1}{n^2} \times 100$$

$$\therefore I_5 = \frac{1}{5^2} \times 100$$

$$I_5 = 4 \text{ A}$$